

1. Simplify the following expressions using postulates and theorems of Boolean algebra.

a) $ABC + A'B + ABC'$

$$AB(C + C') + A'B \quad \text{Postulate 4a (distributive)}$$

$$AB(1) + A'B \quad \text{Postulate 5a}$$

$$AB + A'B$$

$$B(A + A') \quad \text{Postulate 4a (distributive)}$$

$$\boxed{B(1)} \quad \text{Postulate 5a}$$

$$\boxed{B}$$

b) $(BC' + A'D)(AB' + CD')$


$$(BC'AB' + BC'CD' + A'DAB' + A'DCD') \quad \text{Postulate 4a (distributive)}$$

$$C'A(0) + BD'(0) + DB'(0) + A'C(0) \quad \text{Postulate 5b}$$

$$0 + 0 + 0 + 0 \quad \text{Theorem 2}$$

$$\boxed{0}$$

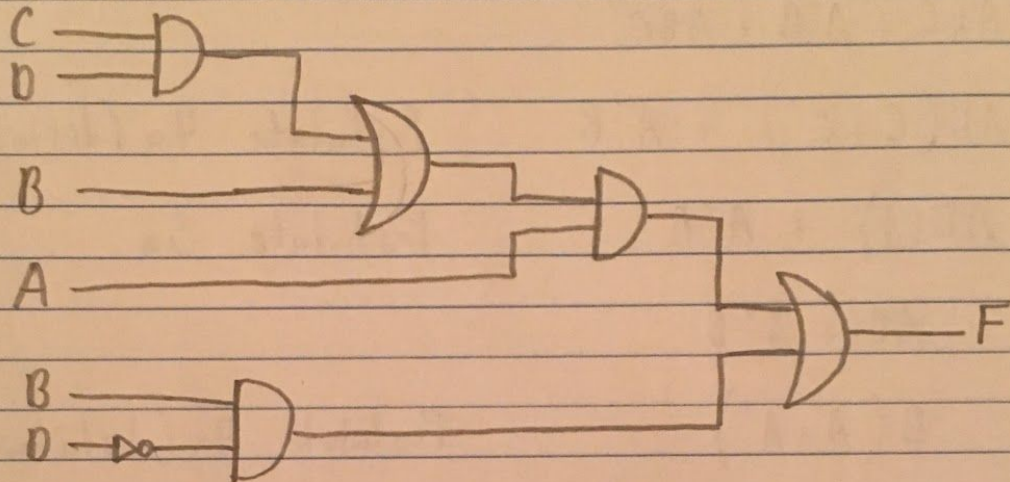2. Implement $F = A(B + CD) + BD'$ in basic gates.



3. Simplify the following Boolean functions using a Karnaugh map.

a) $F(X, Y, Z) = \sum(0, 2, 4, 5, 6)$

X \ YZ	$\bar{Y}\bar{Z}$	$\bar{Y}Z$	$Y\bar{Z}$	YZ
	00	01	11	10
\bar{X} 0	0	1	0	1
X 1	1	1	0	1

$$F(X, Y, Z) = \bar{Z} + X\bar{Y}$$

b) $F(W, X, Y, Z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$

WX \ YZ	$\bar{Y}\bar{Z}$	$\bar{Y}Z$	$Y\bar{Z}$	YZ
	00	01	11	10
$\bar{W}\bar{X}$ 00	0	1	0	1
$\bar{W}X$ 01	4	1	0	1
WX 11	12	1	0	1
$W\bar{X}$ 10	8	1	0	0

$$F(W, X, Y, Z) = \bar{Y} + \bar{W}\bar{Z} + X\bar{Z}$$

$$c) F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

$$F = A'B'C'(1) + B'CD'(1) + A'BCD' + AB'C'(1)$$

Postulate 5a

$$F = A'B'C'(D+D') + B'CD'(A+A') + A'BCD' + AB'C'(D+D')$$

Postulate 4a (distributive)

$$F = A'B'C'D + A'B'C'D' + B'CD'A + B'CD'A' + A'BCD' + AB'C'D + AB'C'D'$$

$$F = \sum(1, 0, 10, 2, 6, 9, 8)$$

AB \ CD	$\overline{C}\overline{D}$ 00		$\overline{C}D$ 01		CD 11		$C\overline{D}$ 10	
	00	01	10	11	00	01	10	11
$\overline{A}\overline{B}$ 00	0	1	1	0	3	0	2	1
$\overline{A}B$ 01	4	0	5	0	7	0	6	1
AB 11	12	0	13	0	15	0	14	0
$A\overline{B}$ 10	8	1	9	1	11	0	10	1

$$F = \overline{B}\overline{C} + \overline{B}\overline{D} + \overline{A}C\overline{D}$$

$$d) F = A'B + BC' + B'C'$$

$$F = A'B(1) + BC'(1) + B'C'(1)$$

Postulate 5a

$$F = A'B(C+C') + BC'(A+A') + B'C'(A+A')$$

Postulate 4a (distributive)

$$F = A'BC + A'BC' + BC'A + BC'A' + B'C'A + B'C'A'$$

$$F = \Sigma(3, 2, 6, 4, 0)$$

	A	BC			
		$\overline{B}\overline{C}$ 00	$\overline{B}C$ 01	$B\overline{C}$ 11	BC 10
\overline{A}	0	0	1	3	2
A	1	4	5	7	6

$$F = \overline{C} + \overline{A}B$$

4) Giving the truth table, derive the canonical SOP and POS

	X	Y	Z	F	
Min 0	0	0	0	1	$\rightarrow \bar{X} \cdot \bar{Y} \cdot \bar{Z}$
Max 1	0	0	1	0	$\rightarrow X + Y + \bar{Z}$
Min 2	0	1	0	1	$\rightarrow \bar{X} \cdot Y \cdot \bar{Z}$
Max 3	0	1	1	0	$\rightarrow X + \bar{Y} + \bar{Z}$
Max 4	1	0	0	0	$\rightarrow \bar{X} + Y + Z$
Max 5	1	0	1	0	$\rightarrow \bar{X} + Y + \bar{Z}$
Max 6	1	1	0	0	$\rightarrow \bar{X} + \bar{Y} + Z$
Min 7	1	1	1	1	$\rightarrow X \cdot Y \cdot Z$

a) Canonical SOP

$$F = (\bar{X} \cdot \bar{Y} \cdot \bar{Z}) + (\bar{X} \cdot Y \cdot \bar{Z}) + (X \cdot Y \cdot Z)$$

$$F = \sum m(0, 2, 7)$$

b) Canonical POS

$$F = (X + Y + \bar{Z})(X + \bar{Y} + \bar{Z})(\bar{X} + Y + Z)(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + Z)$$

$$F = \sum M(1, 3, 4, 5, 6)$$

5. Design a circuit that counts the number of 1's present in 3 inputs A, B, and C. Its output is a two-bit number $X1X0$, representing that count in binary. Assume active-HIGH logic.

a) Truth Table

Input			Number of 1's	Output	
A	B	C		X1	X0
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	2	1	0
1	0	0	1	0	1
1	0	1	2	1	0
1	1	0	2	1	0
1	1	1	3	1	1

b) $2^3 = 8 \rightarrow X1$

A \ BC	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$B\bar{C}$ 11	BC 10
\bar{A} 0			1	
A 1		1	1	1

$$X1 = AC + BC + AB$$

$2^3 = 8 \rightarrow X0$

A \ BC	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$B\bar{C}$ 11	BC 10
\bar{A} 0		1		1
A 1	1		1	

$$X0 = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}\bar{C}$$

c)

A B C

